

ISOLATED FULL BRIDGE DC/DC CONVERTER

1 Abstract

The aim of the work is desinging 96W full-bridge isolating converter with $V_{in} = 12V$ and $V_{out} = 48V$ with 1% output voltage ripple. Switching frequency of the converter is 100kHz.

Contents

Isolated Full Bridge DC/DC Converter	1
1 Abstract	1
2 Circuit Parameters.....	3
3 Magnetic Design.....	10
3.1 Design your transformer with cores which can be found on Magnetics. Clearly indicate the reasoning behind choosing the core. Find the primary and secondary number of turns. Calculate the magnetizing inductance of the transformer. (Hint: Magnetics has some great design guides for inductor and transformer designs. Please have a look at those guidelines.)	11
3.1.1 Number of turns calculations:.....	15
3.1.2 Magnetizing Inductance Calculations:	16
3.1.3 With current density being 4 A/mm ² , find an AWG cable according to the switching frequency and current value. Firstly, calculate the fill factor of the transformer with the chosen cable. Is it a reasonable value? Then, calculate the cable DC and AC resistances and copper loss of the transformer (Proximity can be ignored).....	16
3.1.4 Fill factor calculation:	18
3.1.5 Copper loss calculation:	19

3.1.6	Calculate the core loss of the transformer using core loss formulas given by the manufacturer and compare it with previously found copper loss value. Does your design require new iterations?	20
3.2	Design the output inductor with cores on Magnetics. Find the required number of turns and make sure that core is not saturated by checking the DC bias curves of the material.	20
3.2.1	Compute the product of LI^2 where	21
3.2.2	Number of turns calculation:	22
3.2.3	Choose appropriate AWG cable for the design with 4 A/mm ² current density and calculate the fill factor. Is it a reasonable value? Then, calculate the cable DC and AC resistances and copper loss of the inductor.	23
3.2.4	Copper loss calculation of inductor:.....	23
3.2.5	Calculate the core loss of the inductor and compare it with previously found copper loss value. Does your design require new iterations?	25
4	SIMULATION	26
5	References.....	29

2 Circuit Parameters

- Assuming operating duty cycle is 0.4, find the turns ratio of the transformer.
- Find the required inductance value so that the filter inductor current ripple is 10% of the average inductor current.
- Find the output capacitor value to meet the output voltage ripple requirements. Do not just use the formula, show derivaton.

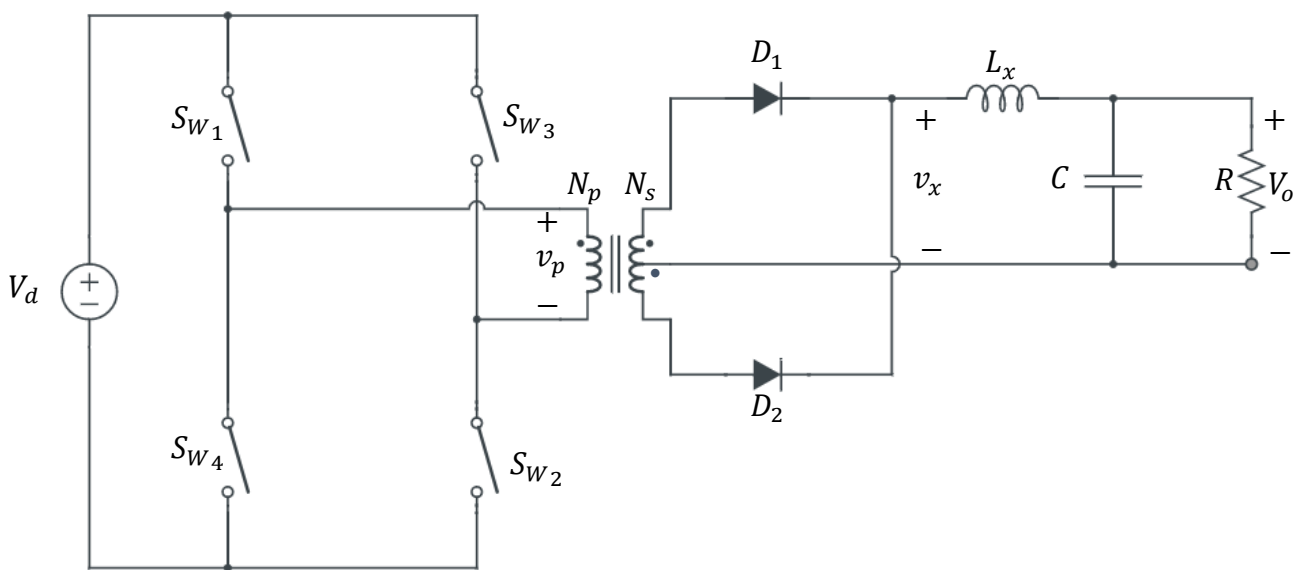


Figure 1. Isolated Full-Bridge Converter

S_{W1} & S_{W2} are operating in simultaneously. Besides, S_{W3} & S_{W4} are operating in simultaneously.

When S_{W1} & S_{W2} are ON and S_{W3} & S_{W4} are OFF:

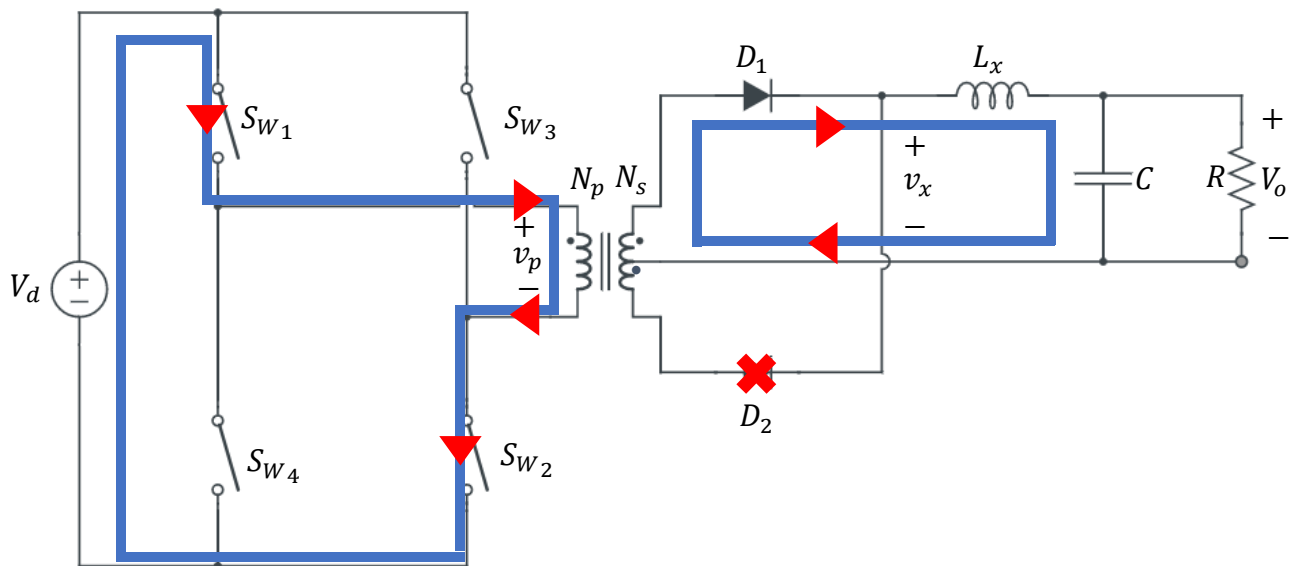


Figure 2. Isolated Full-Bridge SW1 & SW2 ON, SW3 & SW4 OFF

When S_{W1} & S_{W2} are OFF and S_{W3} & S_{W4} are ON:

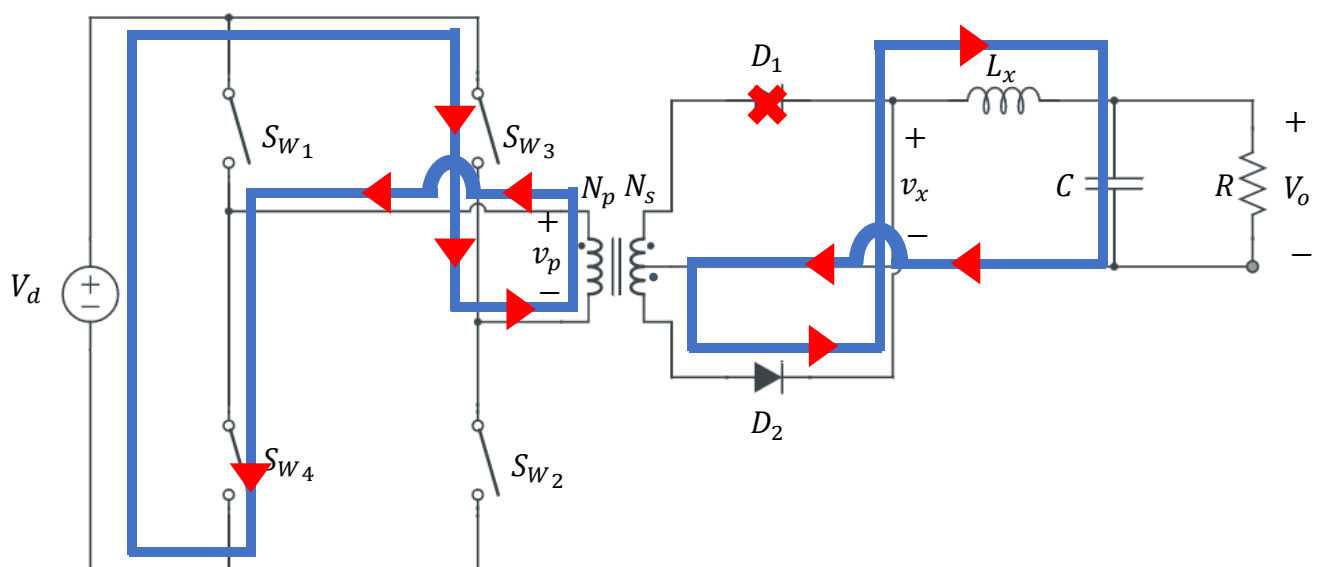


Figure 3. Figure 2. Isolated Full-Bridge SW1 & SW2 OFF, SW3 & SW4 ON

As it can be observed from the figures above, inductor voltage is positive in the both cases, therefore; the third case should be added and it should let discharge the inductor.


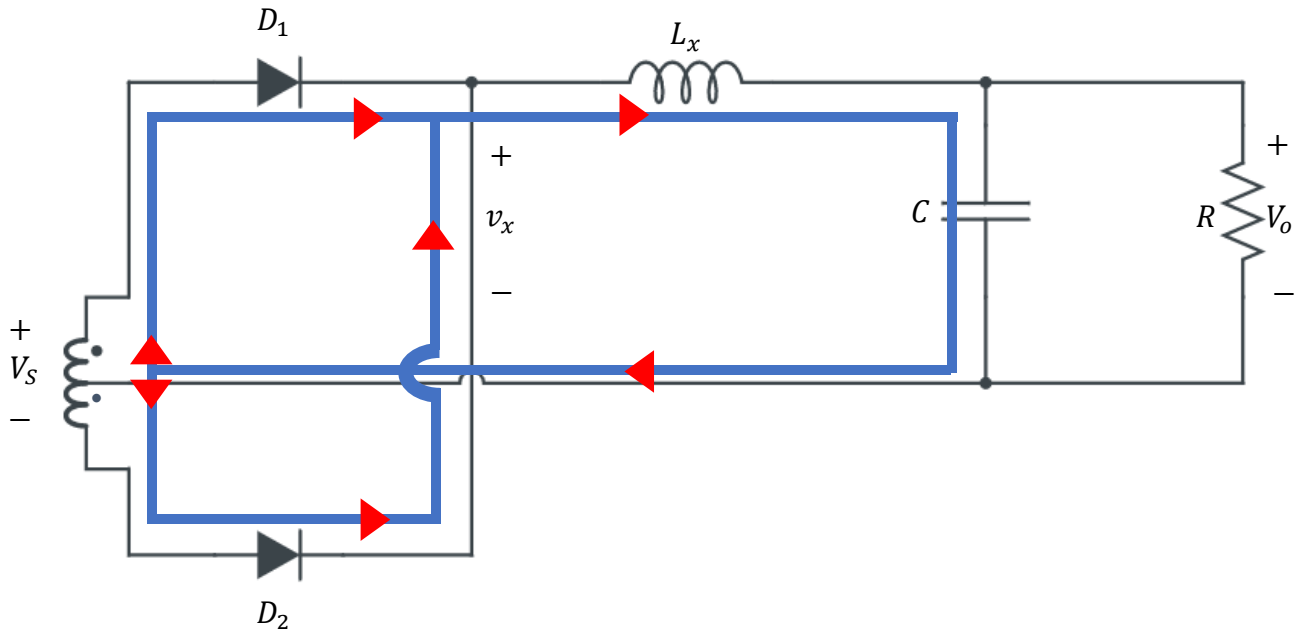


Figure 4. Isolated Full-Bridge SW1, SW2, SW3 & SW4 OFF

Here, voltage induced on secondary side cancels each other and v_{Lx} is being discharged.

$$v_{Lx} = V_s - V_o$$

$$v_{Lx} = -V_o$$

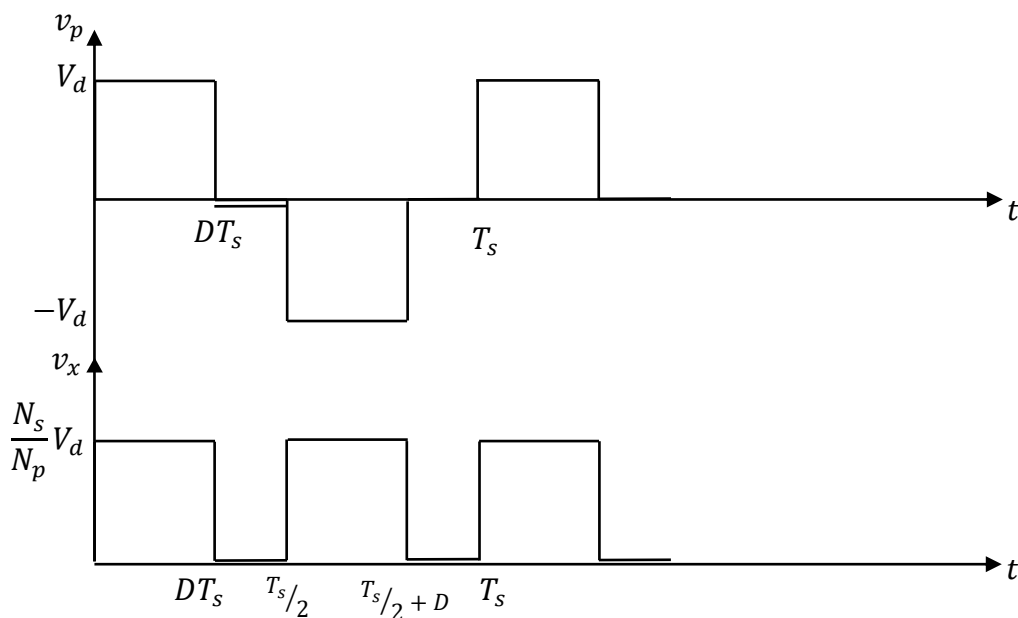

Ripple frequency of inductor current is twice of the main frequency.

As the ripple frequency is twice of main signal.

$$V_o = 2V_d \left(\frac{N_s}{N_p} \right) D$$

The inductor must discharge its energy to not charging up continuously and damage to circuit eventually. There are 2 charge period in the inductor like it can be seen on the graph above. Therefore, duty cycle can't be larger than $D=0.5$. However, there is no discharging period/time; so, D must be smaller than half of the period ($D<0.5$) to discharge properly.

As it is given:

$$V_{in} = 12V$$

$$V_{out} = 48V$$

$$P = 96W$$

$$f_s = 100kHz$$

a) Assuming operating duty cycle is 0.4, find the turns ratio of the transformer.


$$V_o = 2V_d \left(\frac{N_s}{N_p} \right) D$$

$$48 = 2 \times 12 \times \left(\frac{N_s}{N_p} \right) \times 0.4$$

$$\frac{N_s}{N_p} = \frac{48}{9.6} = 5$$

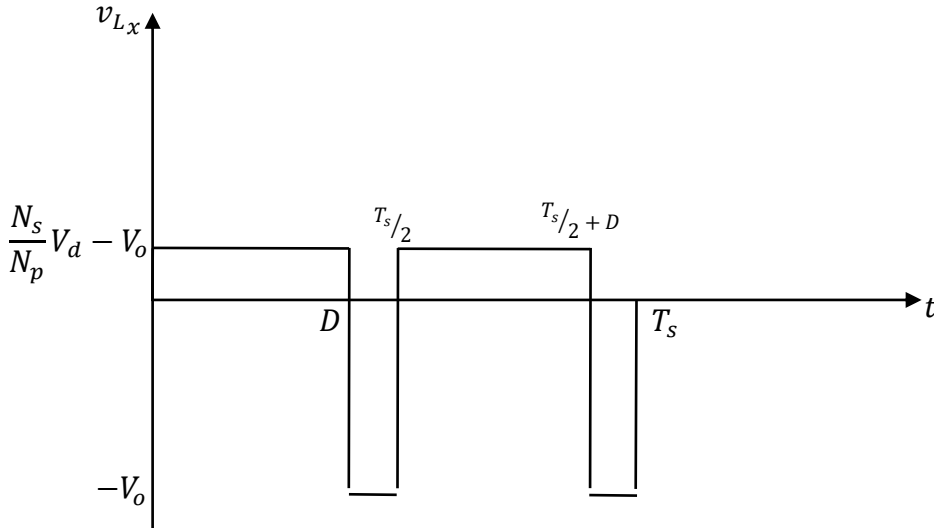- b) Find the required inductance value so that the filter inductor current ripple is 10% of the average inductor current.

To get required inductance value, we need to have voltage waveform of the inductor:



$$v_{Lx} = L \frac{di_{Lx}}{dt} = L \frac{\Delta i_{Lx}}{\Delta T}$$

$$L = \frac{v_{Lx} \times \Delta T}{\Delta i_{Lx}}$$

From the negative portion of the inductor voltage:

$$v_{Lx} = -V_o \text{ and } \Delta T = (0.5 - D)T_s$$

Average inductor current is

$$I_{Lx} = I_o = P_o / V_o = 96W / 48V = 2A$$

$$\Delta i_{Lx} = 0.1 \times 2A = 0.2$$


$$L = \frac{V_o \times (0.5 - D)T_s}{0.2}$$

$$L = \frac{V_o \times (0.5 - D)}{0.2 \times f_s} \text{ where } f_s = 100\text{kHz, and } D = 0.4$$


$$L = \frac{48 \times (0.5 - 0.4)}{0.2 \times 100k} = 240\mu F$$

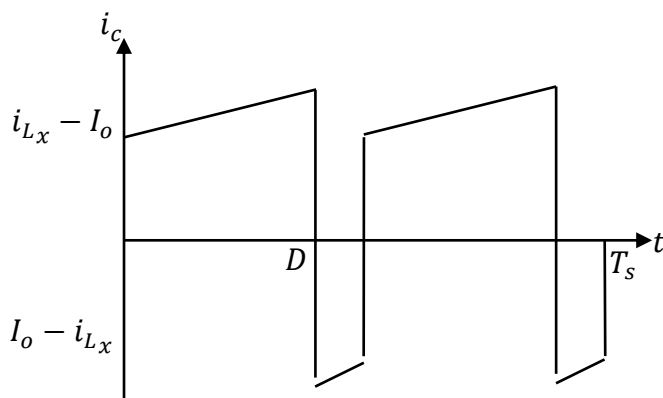- c) Find the output capacitor value to meet the output voltage ripple requirements. Do not just use the formula, show derivaton.

To get required capacitance value, we need to have current waveform of the capacitor:



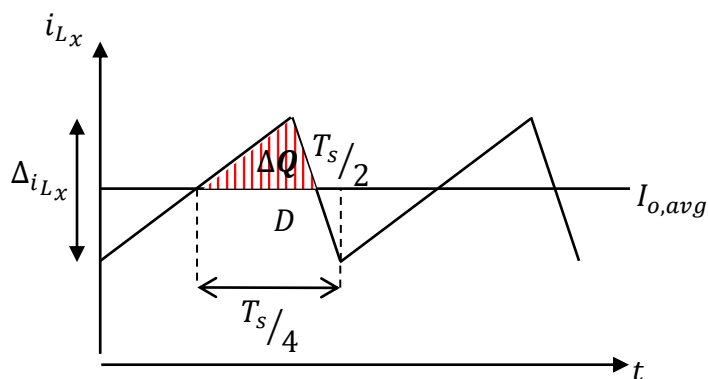It is not easy to calculate capacitance value from this graph. Therefore, it is possible to derive capacitance value from the technique is used in buck converter.



Electrical capacitance says $Q = CV$

$$\Delta Q = C\Delta V$$

$$\Delta Q = \frac{\Delta i_{L_x}/2 \times T_s/4}{2} = \frac{\Delta i_{L_x} \times T_s}{16}$$

$$\Delta V = \frac{\Delta Q}{C}$$

$$\Delta V = \frac{\Delta i_{L_x} \times T_s}{16C}$$

$$\Delta i_{L_x} = \frac{V_{L_x} \times \Delta T}{L_x}$$

Using off-time Δi_{L_x} equation:

$$\Delta i_{L_x} = \frac{V_o \times (0.5 - D)T_s}{L_x}$$

$$\Delta V = \frac{V_o \times (0.5 - D)T_s \times T_s}{16L_x C}$$

$$\Delta V_o = \frac{V_o \times (0.5 - D)T_s^2}{16L_x C} = \frac{V_o \times (0.5 - D)T_s^2}{16L_x C} = \frac{V_o \times (0.5 - D)}{16L_x C f_s^2}$$

$$\frac{\Delta V_o}{V_o} = \frac{(0.5 - D)}{16L_x C f_s^2} \text{ or } \frac{1 - 2D}{32L_x C f_s^2}$$

It is given that we have 1% ripple at the output voltage.

$$0.01 = \frac{1 - 2D}{32L_x C f_s^2} , \text{ where } D = 0.4, L_x = 240\mu F, f_s = 100kHz$$

$$C = 260nF$$

3 Magnetic Design

The total loss of magnetic components -transformer and inductor- should not exceed 15 W and fill factor of the cores should not be less than 30%.

It is strongly advised to use programs such as Matlab or Excel, since magnetic design can be a tedious job which may require a few iterations to find the optimum parameters. A simple script would save you from losing your precious hours.

- a) Design your transformer with cores which can be found on Magnetics. Clearly indicate the reasoning behind choosing the core. Find the primary and secondary number of turns. Calculate the magnetizing inductance of the transformer. (Hint: Magnetics has some great design guides for inductor and transformer designs. Please have a look at those guidelines.)
- b) With current density being 4 A/mm², find an AWG cable according to the switching frequency and current value. Firstly, calculate the fill factor of the transformer with the chosen cable. Is it a reasonable value? Then, calculate the cable DC and AC resistances and copper loss of the transformer (Proximity can be ignored).
- c) Calculate the core loss of the transformer using core loss formulas given by the manufacturer and compare it with previously found copper loss value. Does your design require new iterations?
- d) Design the output inductor with cores on Magnetics. Find the required number of turns and make sure that core is not saturated by checking the DC bias curves of the material.
- e) Choose appropriate AWG cable for the design with 4 A/mm² current density and calculate the fill factor. Is it a reasonable value? Then, calculate the cable DC and AC resistances and copper loss of the inductor.
- f) Calculate the core loss of the inductor and compare it with previously found copper loss value. Does your design require new iterations?

3.1 Design your transformer with cores which can be found on Magnetics. Clearly indicate the reasoning behind choosing the core. Find the primary and secondary number of turns. Calculate the magnetizing inductance of the transformer. (Hint: Magnetics has some great design guides for inductor and transformer designs. Please have a look at those guidelines.)

First, let's try to understand basics:


Faraday's law:

For each turn of wire:

$$v_{turn}(t) = \frac{d\Phi}{dt}$$

Total winding voltage is

$$v(t) = N \frac{d\Phi}{dt}$$

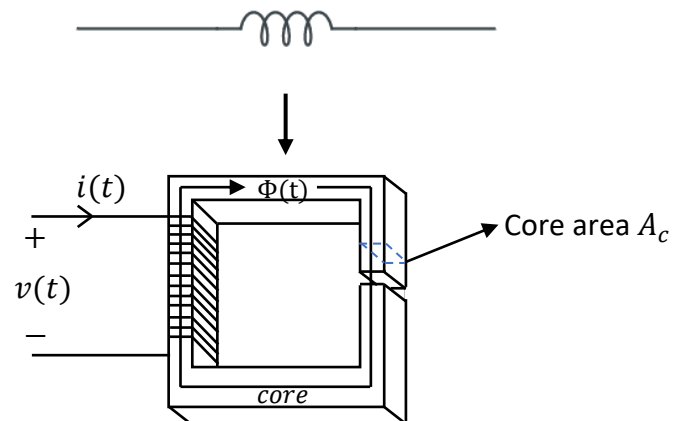

Express flux (Φ) in terms of flux density $\Phi = B_{ac}A_c$

$$V_{pri} = N_{pri}A_c \frac{dB_{ac}(t)}{dt}$$

$$V_{pri} = N_{pri}A_c B_{ac} 2\pi f \frac{2}{\pi}$$

$$V_{pri}I_{pri} = 4N_{pri}A_c B_{ac} f I_{pri}$$

I_{pri} is not one of the specifications of transformer, therefore we can write instead:

$$I = JA_w \quad \text{where } A_w \text{ is the area of copper (wire)}$$

$$V_{pri}I_{pri} = 4N_{pri}A_c B_{ac} f J_{rms} A_w$$

However, A_w is still not related to the transformer specifications, therefore, we can write instead:

$$K_u = \frac{2NA_w}{W_A}$$

$$A_w = \frac{K_u W_A}{2N}$$

Insert A_w into the equation:

$$V_{pri} I_{pri} = 4N_{pri} A_c B_{ac} f J_{rms} A_w$$

$$V_{pri} I_{pri} = 4N_{pri} A_c B_{ac} f J_{rms} \frac{K_u W_A}{2N_{pri}}$$

$$V_{pri} I_{pri} = 2f K_u B_{ac} J_{rms} A_c W_A$$

$$A_c W_A = \frac{V_{pri} I_{pri}}{2K_u J_{rms} B_{ac} f}$$

$$W_A A_c = \frac{P_o D_{cma}}{K_t B_{max} f}$$

Our specifications:

$$P_o = 96W$$

$$K_t \text{ for full-bridge} = 0.0014$$

$$f = 100kHz$$

Suggested interval for D_{cma} is between 500 to 750 cir. mils/amp

$$D_{cma} = 750 \text{ cir. mils/amp}$$

Fill factor K_u

Copper area A_w

Window area W_A

We are using constant 2 because having 2 winding in the transformer

To simplify the equation, following equation can be used which is taken from Magnetics.Inc:

$$W_A A_c = \frac{P_o D_{cma}}{K_t B_{max} f}$$

Where K_t = Topology constant

Forward converter = 0.0005

Push-Pull = 0.001

Half-bridge = 0.0014

Full-bridge = 0.0014

Flyback = 0.00033 (single winding)

Flyback = 0.00025 (multiple winding)

$$D_{cma} = \text{Current density (cir. mils/amp)}$$

Current density can be selected depending upon the amount of heat rise allowed. 750 cir. mils/amp is conservative; 500 cir. mils is aggressive.

B_{max} = Flux Density (gauss) selected based upon frequency of operation. Above 20kHz, core losses increase. To operate ferrite cores at higher frequencies, it is necessary to operate the core flux levels lower than ± 2 kg. The Flux Density vs. Frequency chart shows the reduction in flux levels required to maintain 100 mW/cm³ core losses at various frequencies, with a maximum temperature rise of 25°C. for a typical power material, Magnetics' P material. From [transformer design with magnetics ferrite cores](#) (Mag. Inc)

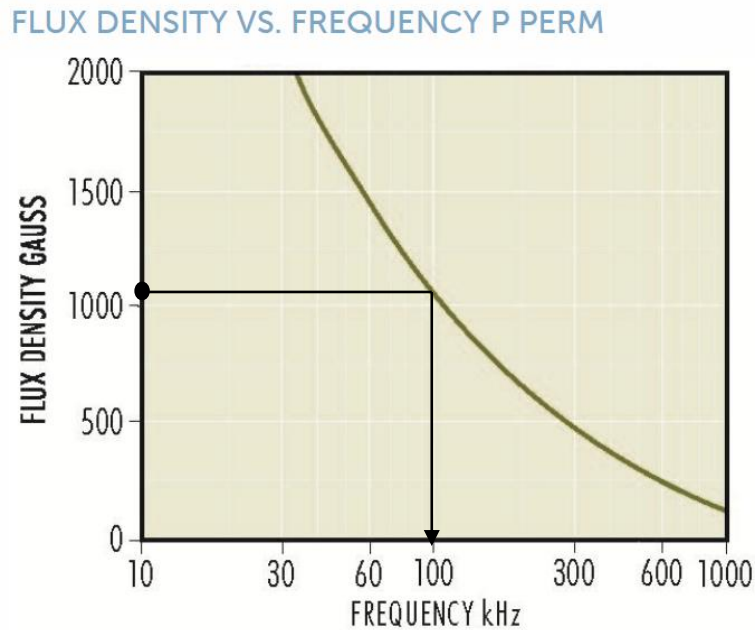


Figure 6. Flux density (gauss) vs frequency (kHz)

From the graph above, it is suitable for using the value $B_{max} = 1000$ (gauss)

$$[Tesla (T) = 10,000 Gauss]$$

$$W_A A_c = \frac{P_o D_{cma}}{K_t B_{max} f}$$

$$W_A A_c = \frac{96 \times 750}{0.0014 \times 1000 \times 100000} = 0.52 (cm^4)$$

Now, it is time to choose suitable core for the design of transformer,

It is important that our core is able to handle power of 96W and meet $W_A A_c = 0.52 (cm^4)$.

When we check [Area Product Distribution \(\$W_A A_c\$ \) Chart \(Mag. Inc\)](#) and [Typical Power Handle Chart \(Mag. Inc\)](#)

$W_A A_c (cm^4)$

0.5		42520 EE 43007 EE	42814 EER		43021 EE				42207 TC	
0.6	43019 DS HS	42515 EE 43009 EE				43618 EE	42823 UG	42625 UG		42220 UU 42515 UU

Figure 7. $W_A A_c$ chart

Suitable cores are 43019 DS HS, 42515 EE, 43009 EE.

20 kHz	50 kHz	100 kHz	250 kHz							
42	70	94	183	43019 HS		42625 PQ			43618 EE	
48	75	108	210	42823 PC 43019 RS DS PC	43009 EE		42512 UU 42515 UU	42929 ETD	44008 EE	42507 TC

Figure 8. Typical power handle chart

We are working on 100kHz. We need at least 96W power ratings for our system. Hence, it is better to choose the bottom row.

Suitable cores are 42823 PC, 43019 RS DS PC, 43009 EE.

43009 EE meets the requirements for $W_A A_c$ and handles the requirement power rating.

Now let's check 43009 EE core in detail. It is a E core with part number 3009.

Part #	AL nH/T2 (nominal)							Le Path Length mm	Ae Cross Section mm ²	Ve Volume mm ³	WaAc cm ⁴	Length mm	Leg Length mm	Height mm
	L 750μ	R 2300μ	P 2500μ	F 3000μ	T 3000μ	J 5000μ	W 10000μ							
3009		2,893	3,147	3,780		5,893		61.9	83.2	5,150	0.59	30.95	13.1	9.4

Figure 9. Magnetics Inc. material list

As it is decided that system will be working on 100mT (1,000 Gauss) and 100kHz.

According to [Magnetics Inc. Ferrite Core Material Summary](#)

The cores have types like L, R, P, F, T

	MATERIAL			L	R	P	F	T
Power Loss (PL) Sine Wave, in mW/cm ³ (typical)		100 kHz 100 mT (1,000 G)	@25°C		87	70	70	65
			@60°C		64	50	65	57
			@100°C		58	65	110	55
			@120°C		64	45	150	58

Figure 10. Ferrite core material types

Power loss of material types can be observed on figure above. To make losses minimize, P or T types are better to use.

The choose is: [P type 3009 E core](#).

3.1.1 Number of turns calculations:

Again from Faraday's law of induction:

$$v(t) = N \frac{d\Phi}{dt}$$

$$V_{pri} = N_{pri} A_c \frac{dB_{ac}(t)}{dt}$$

$$V_{pri} = N_{pri} A_c B_{ac} 2\pi f \frac{2}{\pi}$$

$$V_{pri} = 4N_{pri} A_c B_{ac} f$$

$$N_{pri} = \frac{V_{pri}}{4A_c B_{ac} f} \longrightarrow \text{To simplify the equation, following equation can be used which is taken from Magnetics.Inc:}$$

$$N_p = \frac{V_p}{4BA_c f} 10^8$$

$$V_p = 12V$$

$$B = 1000 \text{ Gauss (100 mT)}$$

$$f = 100 \text{ kHz}$$

$$\text{Effective cross-sectional area } A_e = 83.2 \text{ mm}^2$$

$$N_p = \frac{12}{4 \times 1000 \times 83.2 \times 100000} 10^8 = 3.6 \cong 4 \text{ turns}$$

$$\frac{N_s}{N_p} = 5, \text{ hence } N_s = 20 \text{ turns}$$

3.1.2 Magnetizing Inductance Calculations:

$$L = \frac{N^2}{\mathcal{R}} = A_L N^2$$

$$A_L = \text{inductance factor } 1/\mathcal{R}$$

$$N = \sqrt{L\mathcal{R}} = \sqrt{\frac{L}{A_L}}$$

$$L = A_L N^2$$

$$A_L \text{ value of } \text{OP43009EC} \text{ is } 3147$$

$$L_m = 50.4 \mu H$$

3.1.3 With current density being 4 A/mm², find an AWG cable according to the switching frequency and current value. Firstly, calculate the fill factor of the transformer with the chosen cable. Is it a reasonable value? Then, calculate the cable DC and AC resistances and copper loss of the transformer (Proximity can be ignored).

Cable Selection:

$$I_{sec,rms} = \sqrt{DI_o^2 + 2D(I_o/2)^2} = 1.55 A$$

$$I_{pri,rms} = 12 A$$

Current density J is specified as $4A/mm^2$

Therefore;

$$A_{pri} = 12A/4A/mm^2 = 3mm^2$$

$$A_{sec} = 1.55A/4A/mm^2 = 0.4mm^2$$

Let's check American Wire Gauge(AWG) table:

AWG gauge	Conductor Diameter Inches	Conductor Diameter mm	Conductor cross section in mm ²	Ohms per 1000 ft.	Ohms per km	Maximum amps for chassis wiring	Maximum amps for power transmission	Maximum frequency for 100% skin depth for solid conductor copper	Breaking force Soft Annealed Cu 37000 PSI
0000	0.46	11.684	107	0.049	0.16072	380	302	125 Hz	6120 lbs
000	0.4096	10.40384	84.9	0.0618	0.202704	328	239	160 Hz	4860 lbs
00	0.3648	9.26592	67.4	0.0779	0.255512	283	190	200 Hz	3860 lbs
0	0.3249	8.25246	53.5	0.0983	0.322424	245	150	250 Hz	3060 lbs
1	0.2893	7.34822	42.4	0.1239	0.406392	211	119	325 Hz	2430 lbs
2	0.2576	6.54304	33.6	0.1563	0.512664	181	94	410 Hz	1930 lbs
3	0.2294	5.82676	26.7	0.197	0.64616	158	75	500 Hz	1530 lbs
4	0.2043	5.18922	21.1	0.2485	0.81508	135	60	650 Hz	1210 lbs
5	0.1819	4.62026	16.8	0.3133	1.027624	118	47	810 Hz	960 lbs
6	0.162	4.1148	13.3	0.3951	1.295928	101	37	1100 Hz	760 lbs
7	0.1443	3.66522	10.6	0.4982	1.634096	89	30	1300 Hz	605 lbs
8	0.1285	3.2639	8.37	0.6282	2.060496	73	24	1650 Hz	480 lbs
9	0.1144	2.90576	6.63	0.7921	2.598088	64	19	2050 Hz	380 lbs
10	0.1019	2.58826	5.26	0.9989	3.276392	55	15	2600 Hz	314 lbs
11	0.0907	2.30378	4.17	1.26	4.1328	47	12	3200 Hz	249 lbs
12	0.0808	2.05232	3.31	1.588	5.20864	41	9.3	4150 Hz	197 lbs
13	0.072	1.8288	2.63	2.003	6.56984	35	7.4	5300 Hz	150 lbs
14	0.0641	1.62814	2.08	2.525	8.282	32	5.9	6700 Hz	119 lbs
15	0.0571	1.45034	1.65	3.184	10.44352	28	4.7	8250 Hz	94 lbs
16	0.0508	1.29032	1.31	4.016	13.17248	22	3.7	11 k Hz	75 lbs
17	0.0453	1.15062	1.04	5.064	16.60992	19	2.9	13 k Hz	59 lbs
18	0.0403	1.02362	0.823	6.385	20.9428	16	2.3	17 kHz	47 lbs
19	0.0359	0.91186	0.653	8.051	26.40728	14	1.8	21 kHz	37 lbs
20	0.032	0.8128	0.519	10.15	33.292	11	1.5	27 kHz	29 lbs
21	0.0285	0.7239	0.412	12.8	41.984	9	1.2	33 kHz	23 lbs
22	0.0253	0.64516	0.327	16.14	52.9392	7	0.92	42 kHz	18 lbs
23	0.0226	0.57404	0.259	20.36	66.7808	4.7	0.729	53 kHz	14.5 lbs
24	0.0201	0.51054	0.205	25.67	84.1976	3.5	0.577	68 kHz	11.5 lbs
25	0.0179	0.45466	0.162	32.37	106.1736	2.7	0.457	85 kHz	9 lbs
26	0.0159	0.40386	0.128	40.81	133.8568	2.2	0.361	107 kHz	7.2 lbs
27	0.0142	0.36068	0.102	51.47	168.8216	1.7	0.288	130 kHz	5.5 lbs

Figure 11. American Wire Gauge (AWG) table

$$A_{pri} = 12A/4A/mm^2 = 3mm^2$$

$$A_{sec} = 1.55A/4A/mm^2 = 0.4mm^2$$

In normal conditions, 12AWG for primary, 21AWG for secondary is suitable. But, we have a constraint of skin depth δ . The system switching frequency is 100kHz. As it can be seen on the above list, for both 12AWG and 21AWG, skin depth δ reach maximum value below 100kHz. Therefore, we need to use strands of small gauge which has skin depth δ is above 100kHz. For this purpose, 26AWG cable with having cross-sectional area $0.128mm^2$ is good solution. To get same cross-sectional area, for example, 24×26AWG in parallel for primary winding, 4×26AWG in parallel for secondary windings is necessary.


3.1.4 Fill factor calculation:

$$K_u = \frac{\text{Total copper area}}{\text{Window area}}$$

$$K_u = \frac{A_{w,primary} + 2A_{w,secondary}}{W_A}$$

$$K_u = \frac{3 \times (4 \text{ turns}) + 2 \times 0.4 \times (20 \text{ turns})}{83.2} = 0.34$$

3.1.5 Copper loss calculation:

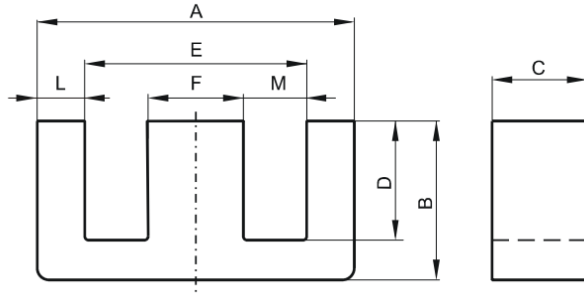

(mm)	Nominal:	Tol. min.:	Tol. max.:
A	30.95	-0.5	+ 0.5
B	13.1	-0.25	+ 0.25
C	9.4	-0.3	+ 0.3
D	8.5 Min.		
E	21.41 Min.		
F	9.4	-0.13	+ 0.13
L	4.29 Nom.		
M	6.0 Min.		
Eff. Parameters			
Ae mm²	Amin mm²	le mm	Ve mm³
83.2	83.2	61.9	5150

Figure 11. OP43009EC core dimensions

$$(MLT) = 2\pi \frac{E - F}{2} = 2\pi \frac{21.41 - 9.4}{2} = 37.73 \text{ mm}$$

$$N_p = 4 \text{ turns}$$

$$R_{pri} = \frac{N_{pri} \times (MLT) \times R_{one \text{ cable}}}{(\text{number of parallel cables})}$$

$$N_s = 20 \text{ turns}$$

Number of parallel cables for pri = 24

$$R_{sec} = \frac{N_{sec} \times (MLT) \times R_{one \text{ cable}}}{(\text{number of parallel cables})}$$

Number of parallel cables for sec = 4

$$R_{pri} = \frac{4 \times 37.73 \times 10^{-3} \times 133.85 \times 10^{-3}}{24} = 0.84 \text{ m}\Omega$$

$$R_{sec} = \frac{20 \times 37.73 \times 10^{-3} \times 133.85 \times 10^{-3}}{4} = 25 \text{ m}\Omega$$

$$P_{cu, total} = I_{pri, rms}^2 R_{pri} + 2 \times I_{sec, rms}^2 R_{sec}$$

$$P_{cu, total} = 12^2 \times 0.84 \text{ m}\Omega + 2 \times 2^2 \times 25 \text{ m}\Omega$$

$$P_{cu, total} = 0.32 \text{ W}$$

3.1.6 Calculate the core loss of the transformer using core loss formulas given by the manufacturer and compare it with previously found copper loss value. Does your design require new iterations?

To calculate core loss, we are using Steinmetz' equation:

$$P_{core} = \alpha f^x B^y V_{core}$$

The parameters depend on the material which is supplied by the manufacturer.

$$V_{core} = 5.150 \text{ mm}^3$$

$$B = 0.1 \text{ T} = (1000 \text{ Gauss})$$

Typically, $1 < x < 3$ and $2 < y < 3$

$$P_{core} = 2 \times 3.53 \times 100000^{1.42} \times (0.1)^{2.88} \times 5.1 = 0.6 \text{ W}$$

$$P_{total} = P_{cu, total} + P_{core} = 0.32 + 0.6 = 0.92 \text{ W}$$

Our system design is not required further iterations. Losses are kind of valid.

3.2 Design the output inductor with cores on Magnetics. Find the required number of turns and make sure that core is not saturated by checking the DC bias curves of the material.

To design an inductor, two parameters must be known:

1. Inductance required with DC bias
2. DC current

Inductance was found as $240 \mu\text{H}$ and DC average current of the inductor is equal to the output current $I_o = 2 \text{ A}$.

The procedure is:

3.2.1 Compute the product of LI^2 where

- L = inductance required with DC bias (millihenries)
- I = maximum DC output current + 1/2 AC Ripple

The ripple is specified as 10%. Therefore, we take I as $2 + (\%10 \times 2)/2 = 2.05A$

$$LI^2 = 240 \times 10^{-6} \times 2.05^2 = 1 \text{ mJ}$$

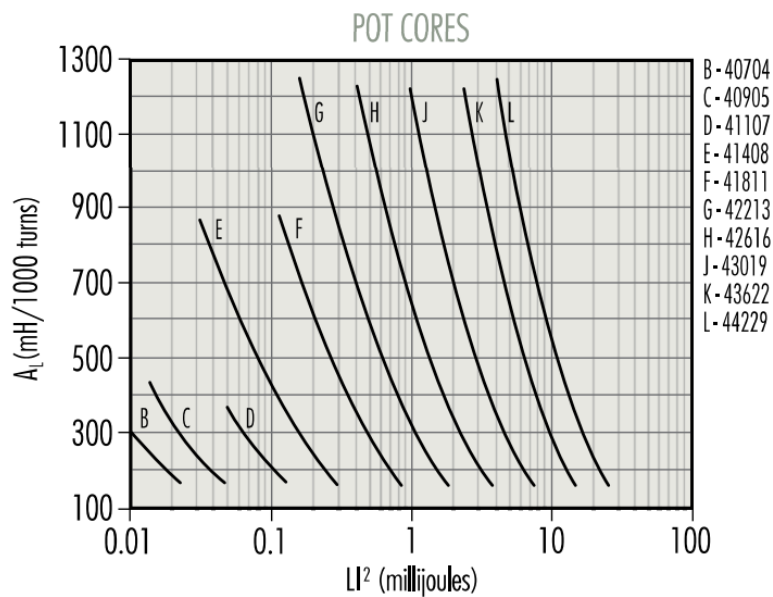


Figure 12. Magnetics Inc. Ferrite core selection chart

From above picture which shows ferrite core selection chart according to LI^2 value.

We found $LI^2 = 1 \text{ mJ}$. Put the value into the chart and follow the coordinate up to intersection point. $A_L (\text{mH}/1000 \text{ turns}) = 300$ and core type is G (42213) which can be found on [Magnetics Inc. Ferrite Pot Cores with part number 2213](#)

Required inductance L , core type and core nominal inductance A_L are known.

3.2.2 Number of turns calculation:

$$N = 10^3 \sqrt{\frac{L}{A_L}}$$

Where L is in millihenries.

$$N = 10^3 \sqrt{\frac{240 \times 10^{-3}}{300}} = 28.28 \cong 29 \text{ turns}$$

Let's recheck

$$L = N^2 A_L \quad (T^2 \times nH/T^2)$$

$$L = 28.28^2 \times 300 \times 10^{-9} = 240 \mu H$$

- d) Design the output inductor with cores on Magnetics. Find the required number of turns and make sure that core is not saturated by checking the DC bias curves of the material.

One of suitable core is Ferrite Pot Core part number 2213 with material type of P, having

$$A_L = 315$$

$$\ell_e (\text{path length}) = 31.5 \text{ mm}$$

$$A_e (\text{cross-sectional area}) = 63.4 \text{ mm}^2$$

To check saturation:

The maximum allowable H = 25 Oersted

$$\ell_e (\text{path length}) \text{ in cm} = 3.15 \text{ cm}$$

$$NI (\text{maximum}) = 0.8 \times H \times \ell_e$$

$$NI \text{ (maximum)} = 0.8 \times 25 \times 3.15 \text{ cm} = 63 \text{ A} \cdot \text{T}$$

So, it is in safe region.

3.2.3 Choose appropriate AWG cable for the design with 4 A/mm² current density and calculate the fill factor. Is it a reasonable value? Then, calculate the cable DC and AC resistances and copper loss of the inductor.

We have 2.2A passing through the inductor.

$$A_{\text{inductor}} = 2.2 \text{ A} / 4 \text{ A/mm}^2 = 0.54 \text{ mm}^2$$

From AWG list in page 16, 19AWG with 0.653 mm^2 is suitable; however, skin depth factor is occurs because our system is working on 100kHz.

Therefore, we can use parallel strands 26AWG with 0.128 mm^2 by the number of 5. Therefore, core losses can be minimized.


3.2.4 Copper loss calculation of inductor:

$$R_{\text{inductor}} = \frac{N_{\text{inductor}} \times (MLT) \times R_{\text{one cable}}}{(\text{number of parallel cables})}$$

$$R_{\text{one cable}} = 133.8568 \times 10^{-3} \Omega \text{ for 26AWG}$$

$$N_{\text{inductor}} = 29 \text{ turns}$$

DIMENSIONS

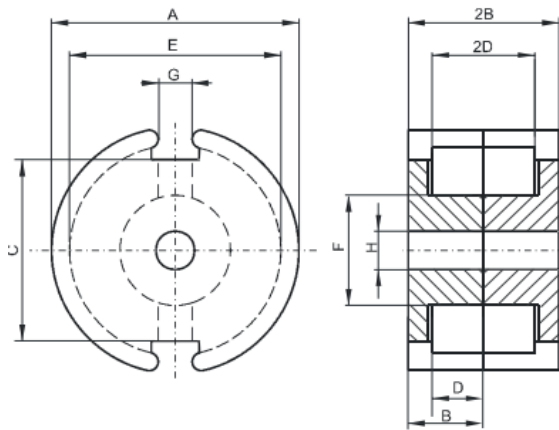

(mm)	Nominal:	Tol. min.:	Tol. max.:
A	22.0	-0.8	0.0
B	6.7	-0.1	+ 0.1
2B	13.4	-0.2	+ 0.2
C	15.0	-0.4	+ 0.4
D	4.6	0.0	+ 0.2
2D	9.2	0.0	+ 0.4
E	17.9	0.0	+ 0.6
F	9.4	-0.3	0.0
G	3.8	-0.6	+ 0.6
H	4.4	0.0	+ 0.3
Eff. Parameters			
Ae mm²	Amin mm²	le mm	Ve mm³
63.4	50.9	31.5	2000

Figure 13. POT core dimensions

$$(MLT) = 2\pi \frac{E - G}{2} = 2\pi \frac{17.9 - 3.8}{2} = 44.3mm$$

$$R_{inductor} = \frac{29 \times 44.3 \times 10^{-3} \times 133.8568 \times 10^{-3}}{5} = 34.4m\Omega$$

Copper loss of inductor

$$P_{cu} = I_L^2 R_{inductor}$$

$$P_{cu} = 2.2^2 \times 34.4m\Omega = 0.17W$$

3.2.5 Calculate the core loss of the inductor and compare it with previously found copper loss value. Does your design require new iterations?

Core loss calculation of inductor:

$$P_{core}(mW) = \alpha f^x B^y V_e$$

$$V_e = 2000mm^3$$

$$f = 100kHz$$

Typically, $1 < x < 3$ and $2 < y < 3$

$$P_{core} = 3.53 \times 100000^{1.42} \times 0.1^{2.9} \times 2 = 0.1W$$

$$P_{total} = P_{core} + P_{cu} = 0.17 + 0.1 = 0.27W$$

All values seems to be valid.

4 SIMULATION

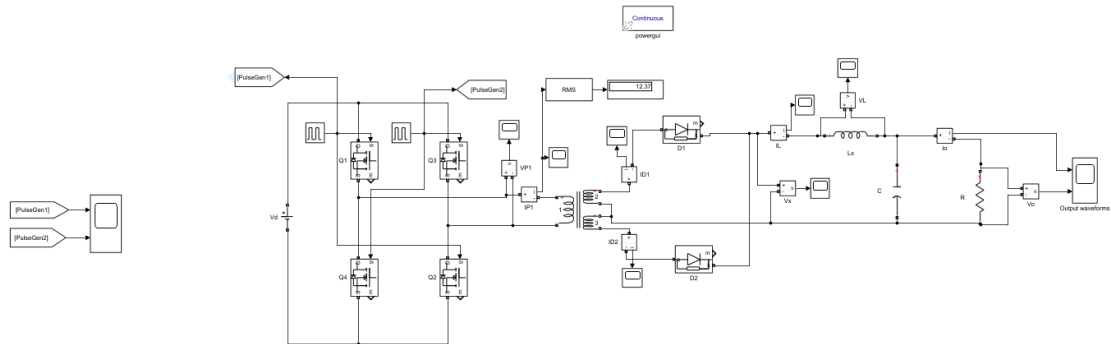


Figure 14. Simulink schematic design of Full-Bridge DC-DC Converter

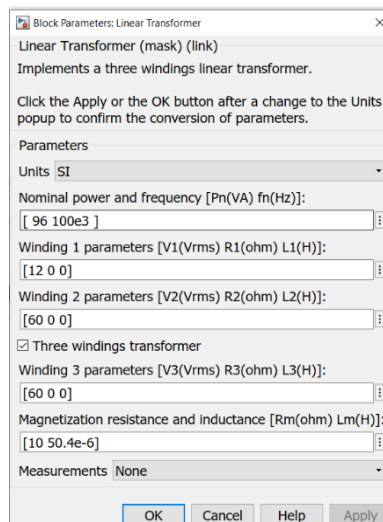


Figure 15. Transformer parameters

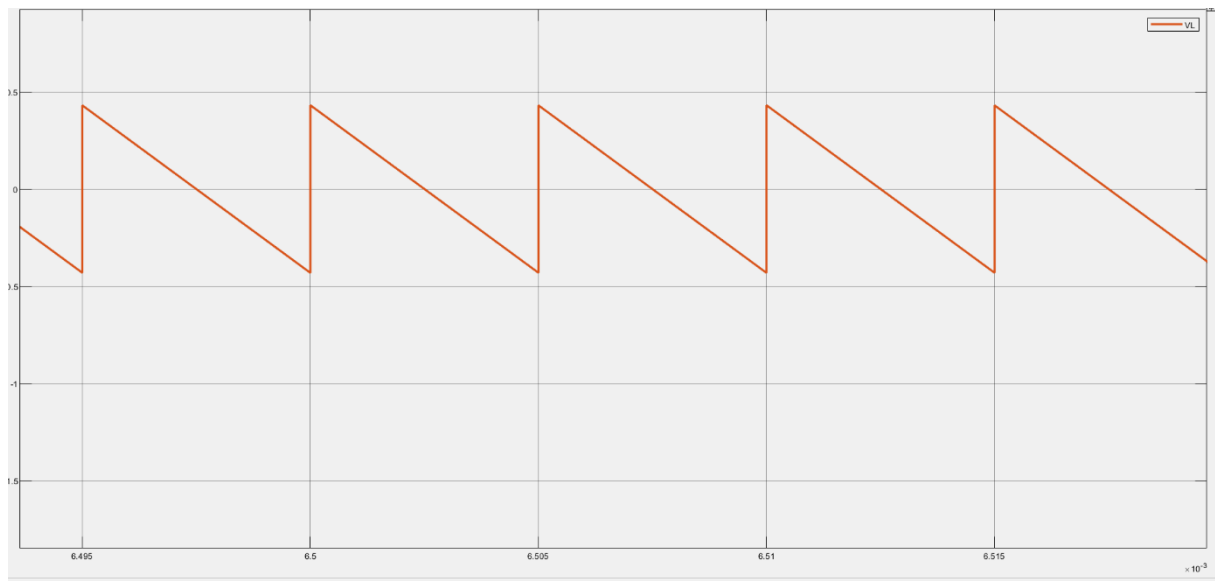


Figure 16. Inductor voltage waveform

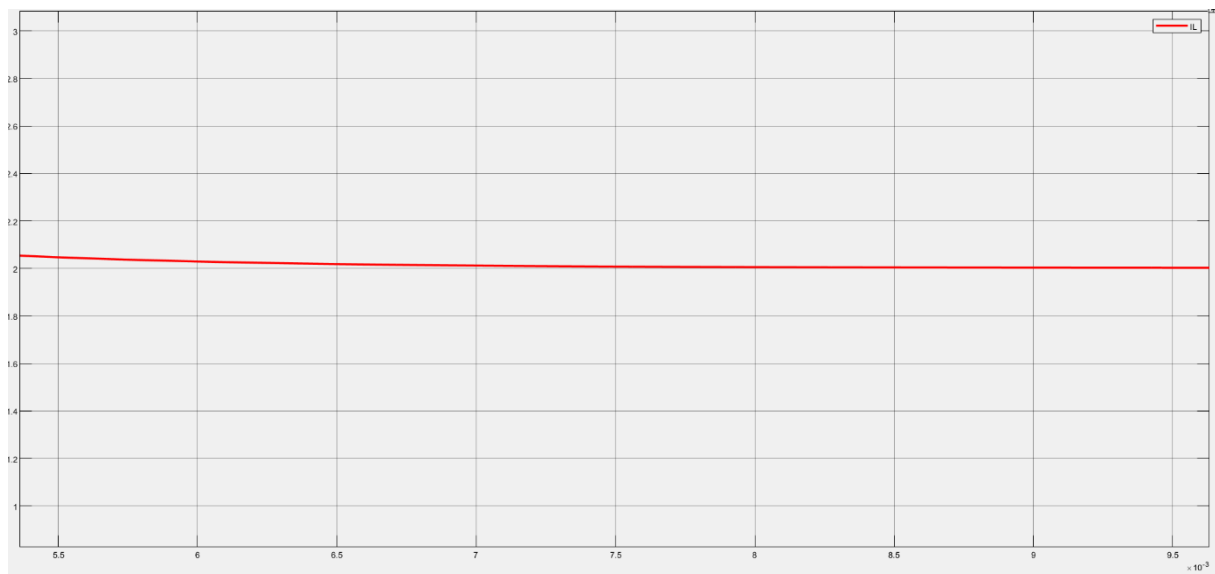


Figure 17. Inductor current waveform

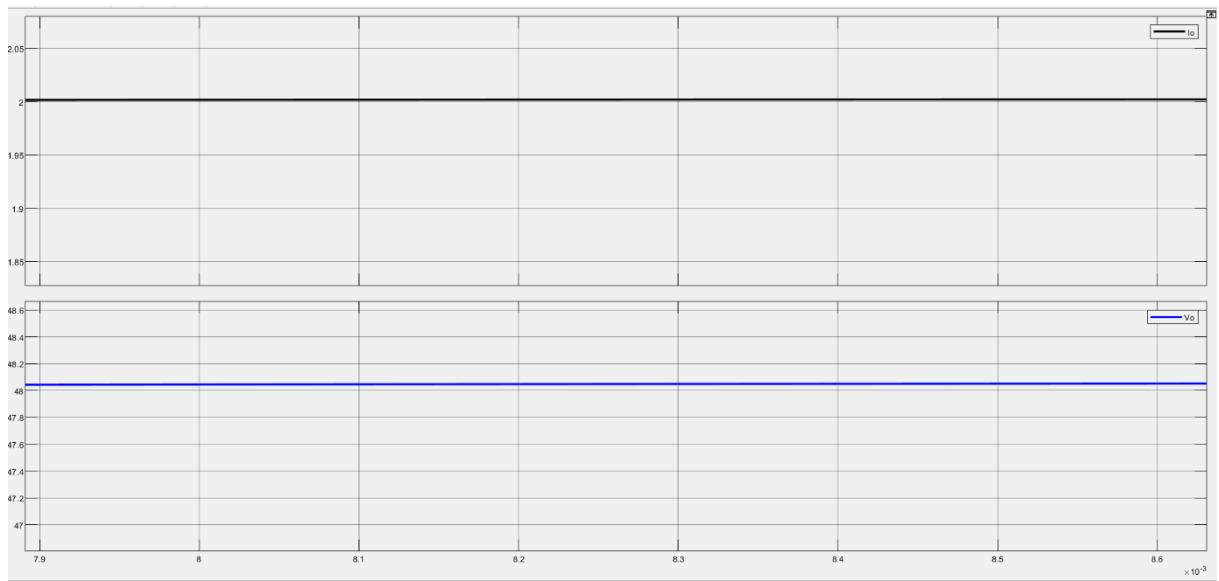


Figure 18. Output parameters

5 References

- [1] (n.d.). *Magnetic Design Guides*. Magnetics. <https://www.mag-inc.com/Design/Design-Guides>